

Lab 3: Loading Effect of Voltage Divider Circuit

Objective:

- To analyze how the voltage divider circuit behaves when there is no load resistance connected.
- Evaluate the performance of voltage divider circuit due to loading.

List of Equipment:

- Trainer Board
- DMM
- $2 \times 560\Omega$ resistors
- $1 \times (0-10k\Omega)$ variable resistor

Introduction:

Voltage Divider circuit provides a simple way to convert a DC voltage to another lower DC voltage.

Consider the following voltage divider circuit.

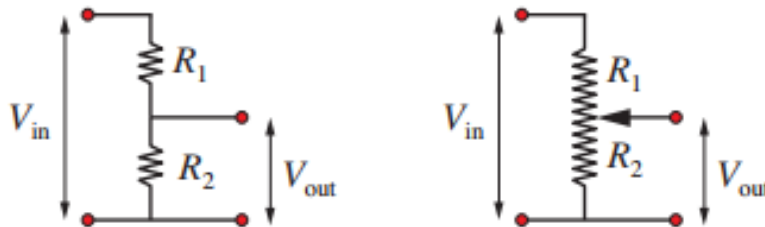



Figure 1: A voltage divider on the left, and potentiometer on the right.

The voltage drop across R_2 is the output voltage, V_{out} . V_{out} is less than V_{in} because the total voltage across R_1 and R_2 must add up to V_{in} . A potentiometer can also be used to change V_{out} by changing the resistance R_2 . As the value of R_2 is changed, it allows the output voltage to be adjusted from 0 to V_{in} .

In Figure 1, there is no output load (R_L) connected in parallel to R_2 hence we call it a No-Load circuit.

According to Voltage Divider Rule: $V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$ (1)

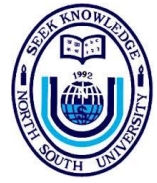- Say $V_{in}=5v$ and you need $V_{out}= 3v$. How would you set the values of R_1 and R_2 ?



$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$

Choice of resistor value should follow the ratio: $\frac{R_1}{R_2} = \frac{2}{3}$

One possible combination: $R_1 = 2k$ and $R_2 = 3k$

- Now say we connect an output load, R_3 in parallel to R_2 :

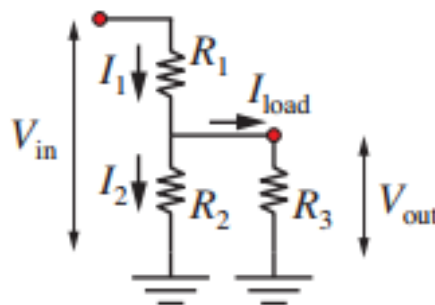


Figure 2: With Output Load Connected.

⇒ Do you think keeping the values of resistors same would still give $V_{out} = 3v$ from $V_{in} = 5v$?
Let's check:

Since you have a Load resistance parallel to R_2 , your Voltage divider formula to find V_{out} is:

$$V_{out} = V_{in} \frac{(R_2 // R_3)}{R_1 + (R_2 // R_3)} \quad (2)$$

Let $R_3 = 10k$.

$$R_2 // R_3 = 2.31k$$

$$\rightarrow V_{out} = 2.68 v$$


So, our Designed value was 3v, but connecting a load resistor reduced it to 2.68v.

Design Criteria:

To minimize the loading effect, choose the load resistor to be much larger than its parallel resistor.

If R_3 is much greater than R_2 then $R_2 // R_3$ (parallel combination of R_2 and R_3) is approximately equal to R_2

Circuit Diagram:

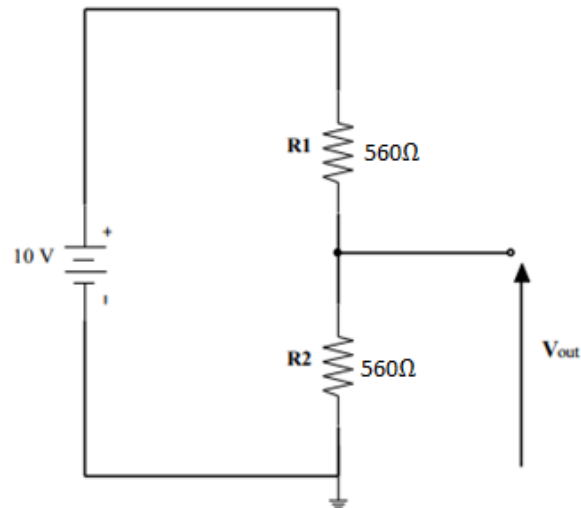

Procedure:

1. Construct the voltage divider circuit as shown in figure above.
2. Measure the unloaded output voltage V_{out} . Record the value in Table 1.
3. Connect 10 kΩ variable load resistor, parallel with R2 to the circuit. (Connect 1 middle pin of variable resistor and one of the other pins).
4. Change the value of the variable resistor according to Table 1, and record V_{out} for each resistor value in Table 1.



Data Collection for Lab 3:

Group No. _____ Instructor's Signature _____

Table 1:

RL	Vout (Measured)	Vout (Calculated)	%Error
No resistor			
1k			
4k			
7k			
10k			

Report Question:

1. Explain the loading effect of your circuit (i.e explain how does your Vout vary with increasing Load resistor)
2. Showing all steps in details, theoretically calculate the value of Vout for each load resistor.
3. Comparing the theoretical data to the experimental data, comment how far the loading effect of your circuit supports the theory.